

LABORATORY NO. 9:
SIMPLE CALCULATOR (FINAL LAB)

By: Derek Hildreth

Instructor: Brother Fisher

BYU-Idaho CompE 340

July 16, 2009

I. INTRODUCTION

A. Purpose

Students will combine the sub-modules that were created in the previous lab exercises to complete the `SIMPLE_CALC` module. They will also use a Verilog generate statement to choose between the two versions of the `COMP` module. Students will develop a test bench that thoroughly verifies the structural module. They will also modify the `ROM` contents to hold the specific values that you will use in the verification process. Finally, they will implement the logic, targeting the Spartan-3 FPGA, and examine the contents of the report files.

The schematic for the calculator is shown in Figure 4 below. Students will write the RTL description for the top-level module `SIMPLE_CALC`.

B. Equipment

There is a minimal amount of equipment to be used in this lab. The few requirements are listed below:

- Xilinx ISE Navigator Software (v10.0.1)
- Spartan 3E Developer Board
- Computer capable of running the software mentioned

C. Procedure

1. Start the ISE Navigator.
2. Create a new project.
3. Import the `.v` source files for the `MEM`, `COMP_BEH`, `COMP_RTL`, `ALU` and `CNTRL_FSM` sub-modules
4. Modify the source code for the `MEM` module, updating the `ROM` contents by using the data that you recorded earlier for the `ALU` verification.
5. Write Verilog code and check syntax for the `SIMPLE_CALC` module.
6. Create generate statements that choose either the `COMP_BEH` or `COMP_RTL` sub-modules. Recall that the `COMP_BEH` module is written in a behavioral style – intended only for simulation – and that the `COMP_RTL` module is written in an RTL style for synthesis.
7. Perform a syntax check.
8. Create a test bench for `SIMPLE_CALC` and run a simulation to verify functionality.
9. Implement (Place & Route) the design and examine the contents of the `MAP` and `PAR` report files.

II. SCHEMATIC DIAGRAMS

This section consists of block diagrams which are useful for the laboratory procedure as well as simulation results.

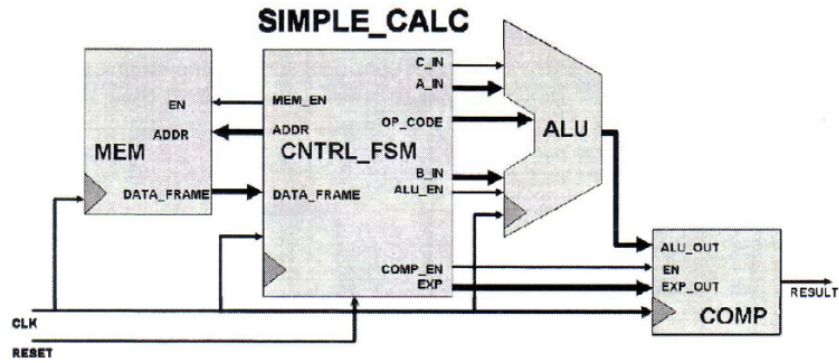


FIG. 1: Overall block diagram of the calculator project showing the relationship of all of the components.



FIG. 2: RTL view for the simple calculator.

 


FIG. 3: Detailed RTL view for the simple calculator with all modules.

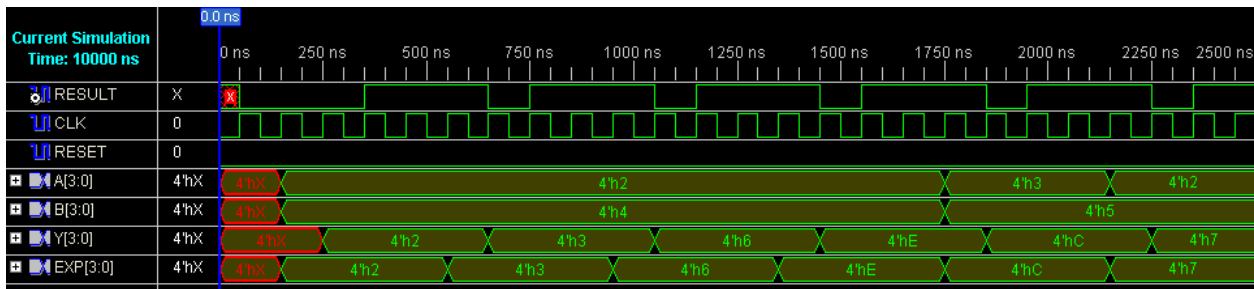


FIG. 4: Simulation results for the entire simple calculator.

III. EXPERIMENT DATA

This section will consist of the code blocks that created the counter block as seen in Figure 4.

A. Main Simple Calculator Module

This is the verilog simple calculator file called (SIMPLE_CALC.v).

```
'timescale 1ns / 1ps
'define SYNTH 1
module SIMPLE_CALC(
    input CLK,
    input RESET,
    output RESULT
);
    wire [3:0] A_IN, B_IN, OP_CODE, EXP_OUT, ALU_OUT;
    wire C_IN, MEM_EN, COMP_EN, ALU_EN;
    wire [2:0] ADDR;
    wire [16:0] DATA_FRAME;

    ALU U0(.A(A_IN), .B(B_IN), .C_IN(C_IN), .OP_CODE(OP_CODE), .CLK(CLK), .EN(ALU_EN), .Y(ALU_OUT));
    CNTRLFSM U2(.RESET(RESET), .CLK(CLK), .DATA_FRAME(DATA_FRAME), .A_IN(A_IN), .B_IN(B_IN), .C_IN(C_IN), .OP_CODE(OP_CODE),
    .EXP(EXP_OUT), .ALU_EN(ALU_EN), .MEM_EN(MEM_EN), .COMP_EN(COMP_EN), .ADDR(ADDR));
    MEM U3(.ADDR(ADDR), .DATA_FRAME(DATA_FRAME), .CLK(CLK), .EN(MEM_EN));

    generate
    if (SYNTH)
        //COMP_RTL U4(COMP_EN, EXPECTED, ALU_OUT, CLK, RESULT);
        COMP_RTL U4(.COMP_EN(COMP_EN), .EXPECTED(EXP_OUT), .ALU_OUT(ALU_OUT), .CLK(CLK), .RESULT(RESULT));
    else
        //COMP_BEH U5(COMP_EN, EXPECTED, ALU_OUT, CLK, RESULT);
        COMP_BEH U5(.COMP_EN(COMP_EN), .EXPECTED(EXP_OUT), .ALU_OUT(ALU_OUT), .CLK(CLK), .RESULT(RESULT));
    endgenerate
endmodule
```

This is the text fixture for the simple calculator called (SIMPLE_CALC.TB.v).

```
'timescale 1ns / 1ps
module SIMPLE_CALC_TB;
    // Inputs
    reg CLK;
    reg RESET;

    // Outputs
    wire RESULT;

    // Instantiate the Unit Under Test (UUT)
    SIMPLE_CALC uut (
        .CLK(CLK),
        .RESET(RESET),
        .RESULT(RESULT)
    );

    initial begin
        // Initialize Inputs
        CLK = 0;
        RESET = 0;

        #1 RESET = 1;
        #1 RESET = 0;

        // Wait 100 ns for global reset to finish
        #100;
    end

    always
        #50 CLK = ~CLK;
endmodule
```

This is the pin out information for the hardware simple calculator called Full.ucf.

```
#PACE: Start of Constraints generated by PACE
#This ucf file has all the switches and LEDs that might be used in CompE 224
```

```

#Modify this file with your net names and comment out or delete the lines not needed.
#PACE: Start of PACE I/O Pin Assignments

#Main Switches
#NET "SW3" LOC = "N17" ;
#NET "SW2" LOC = "H18" ;
#NET "SW1" LOC = "L14" ;
#NET "SW0" LOC = "L13" ;

#Extra Switches
#NET "SW7" LOC = "A6" ;
#NET "SW6" LOC = "B6" ;
#NET "SW5" LOC = "E7" ;
#NET "SW4" LOC = "F7" ;

#Main LED's
NET "RESULT" LOC = "F9" ;
#NET "LED6" LOC = "E9" ;
#NET "LED5" LOC = "D11" ;
#NET "LED4" LOC = "C11" ;
#NET "LED3" LOC = "F11" ;
#NET "LED2" LOC = "E11" ;
#NET "LED1" LOC = "E12" ;
#NET "LED0" LOC = "F12" ;

#Extra LED's
#NET "LED11" LOC = "B4" ;
#NET "LED10" LOC = "A4" ;
#NET "LED9" LOC = "D5" ;
#NET "LED8" LOC = "C5" ;

#Pushbutton Switches
#NET "BTN_North" LOC = "V4" | PULLDOWN ;
NET "RESET" LOC = "H13" | PULLDOWN ; # East
NET "CLK" LOC = "K17" | PULLDOWN ; #South
#NET "BTN_West" LOC = "D18" | PULLDOWN ;

NET "CLK" CLOCK_DEDICATED_ROUTE = FALSE;

#Debouncer C9.50MHz
#NET "CLK" LOC = "C9" ;

#Used for correction of error with refrence to none dedicated clock inputs
#Need to input the net name in place of switch inside the "
#NET "switch" CLOCK_DEDICATED_ROUTE = FALSE;

#PACE: Start of PACE Area Constraints
#PACE: Start of PACE Prohibit Constraints
#PACE: End of Constraints generated by PACE

```

This is the map report for the simple calculator called Map_Report.txt.

```

Release 10.1.02 Map K.37 (nt)
Xilinx Mapping Report File for Design 'SIMPLE_CALC'

Design Information

Command Line : map -ise C:/CompE340/Lab09/Lab09.ise -intstyle ise -p
xc3s500e-fg320-4 -cm area -pr off -k 4 -c 100 -o SIMPLE_CALC.map.ncd
SIMPLE_CALC.ngd SIMPLE_CALC.pcf
Target Device : xc3s500e
Target Package : fg320
Target Speed : -4
Mapper Version : spartan3e -- $Revision: 1.46.12.2 $
Mapped Date : Wed Jul 15 20:20:56 2009

Design Summary

Number of errors: 0
Number of warnings: 1
Logic Utilization:
  Number of Slice Flip Flops: 20 out of 9,312 1%
  Number of 4 input LUTs: 40 out of 9,312 1%
Logic Distribution:
  Number of occupied Slices: 23 out of 4,656 1%
  Number of Slices containing only related logic: 23 out of 23 100%
  Number of Slices containing unrelated logic: 0 out of 23 0%
  *See NOTES below for an explanation of the effects of unrelated logic.
Total Number of 4 input LUTs: 40 out of 9,312 1%
Number of bonded IOBs: 3 out of 232 1%
Number of BUFGMUXs: 1 out of 24 4%

Peak Memory Usage: 153 MB
Total REAL time to MAP completion: 6 secs
Total CPU time to MAP completion: 3 secs

!--- RESULTS SNIPPED FOR LAB REPORT ---!

```

B. Individual Modules

This is alu.v.

```
'timescale 1ns / 1ps

module ALU(
    input [3:0] A,
    input [3:0] B,
    input C_IN,
    input [3:0] OP_CODE,
    input CLK,
    input EN,
    output reg [3:0] Y
);

always @ (posedge CLK)
    if (EN)
        begin
            case (OP_CODE) // Specify outputs for each address.
                4'b0000:
                    Y = A + C_IN;
                4'b0001:
                    Y = A + B + C_IN;
                4'b0010:
                    Y = A + (~B) + C_IN;
                4'b0011:
                    Y = A - 1 + C_IN;
                4'b0100:
                    Y = A & B;
                4'b0101:
                    Y = A | B;
                4'b0110:
                    Y = A ^ B;
                4'b0111:
                    Y = ~A;
                4'b1000:
                    Y = 0;
                default:
                    Y = 0;
            endcase
        end
endmodule
```

This is CNTRL_FSM.v.

```
'timescale 1ns / 1ps

module CNTRLFSM(
    input RESET,
    input CLK,
    input [16:0] DATA_FRAME,

    output reg [16:13] A_IN,
    output reg [12:9] B_IN,
    output reg C_IN,
    output reg [7:4] OP_CODE,
    output reg [3:0] EXP,

    output reg ALU_EN,
    output reg MEM_EN,
    output reg COMP_EN,
    output reg [2:0] ADDR
);

localparam [4:0]
    S0_INIT = 5'b00001,
    S1_FETCH = 5'b00010,
    S2_ALU = 5'b00100,
    S3_COMP = 5'b01000,
    S4_DONE = 5'b10000; // Explicite make sure condition to stay in state

reg [4:0] CURR_STATE;
reg [4:0] NEXT_STATE;
reg [2:0] ADDR_I; // used to increment ADDR internally.

always @ (posedge CLK, posedge RESET) // current state proc block
begin
    // $display ("Current State: %b @ ADDR_I: %d", CURR_STATE, ADDR_I);
    if (RESET == 1'b1) // if reset asserted
        begin
            CURR_STATE <= S0_INIT; // Reset to state 0
            ADDR <= 3'b000;
        end
    else
        begin
            CURR_STATE <= NEXT_STATE; // goto next state
            ADDR <= ADDR_I;
        end
    end
end

always @ (CURR_STATE)
begin
    A_IN = DATA_FRAME[16:13];
    B_IN = DATA_FRAME[12:9];
end
```

```

C_IN = DATA_FRAME[8];
OP_CODE = DATA_FRAME[7:4];
EXP = DATA_FRAME[3:0];

ADDR_I = ADDR; // assignment prevents latch inference.

case (CURR_STATE)
  S0_INIT:
    begin
      ALU_EN = 1'b0;
      MEM_EN = 1'b0;
      COMP_EN = 1'b0;

      NEXT_STATE = S1_FETCH;
    end
  S1_FETCH:
    begin
      ALU_EN = 1'b0;
      MEM_EN = 1'b1;
      COMP_EN = 1'b0;

      NEXT_STATE = S2_ALU;
    end
  S2_ALU:
    begin
      ALU_EN = 1'b1;
      MEM_EN = 1'b0;
      COMP_EN = 1'b0;

      NEXT_STATE = S3_COMP;
    end
  S3_COMP:
    begin
      ALU_EN = 1'b0;
      MEM_EN = 1'b0;
      COMP_EN = 1'b1;

      NEXT_STATE = S4_DONE;
    end
  S4_DONE:
    begin
      ALU_EN = 1'b0;
      MEM_EN = 1'b0;
      COMP_EN = 1'b0;

      if (ADDR_I >= 3'b101)
        begin
          NEXT_STATE = S4_DONE;
        end
      else
        begin
          NEXT_STATE = S1_FETCH;
          ADDR_I = ADDR_I + 1;
        end
      end
    end
  default:
    begin
      ALU_EN = 1'b0;
      MEM_EN = 1'b0;
      COMP_EN = 1'b0;

      NEXT_STATE = S0_INIT;
    end
endcase
end
endmodule

```

This is comp_beh.v.

```

`timescale 1ns / 1ps

module COMP_BEH(
  //INPUTS
  input wire COMP_EN, // 1-bit - enable wire from FSM
  input wire [3:0] EXPECTED, // 4-bit - expected output, loaded from ROM
  input wire [3:0] ALU_OUT, // 4-bit - actual output from ALU
  input wire CLK, // 1-bit - clock input

  //OUTPUTS
  output reg RESULT // 1-bit - result of comparison
);

always @ (posedge CLK)
begin
  assign RESULT = EXPECTED == ALU_OUT;

  if (!RESULT)
    $display("At_time_%t,_EXP_=%b,_ACT_=%b,_RESULT_=%b", $time, EXPECTED, ALU_OUT, RESULT);
end
endmodule

```

This is comp_rtl.v.

```

`timescale 1ns / 1ps

```



```

module COMP_RTL(
  //INPUTS
  input wire COMP_EN, // 1-bit - enable wire from FSM
  input wire [3:0] EXPECTED, // 4-bit - expected output, loaded from ROM
  input wire [3:0] ALU_OUT, // 4-bit - actual output from ALU
  input wire CLK, // 1-bit - clock input

  //OUTPUTS
  output reg RESULT // 1-bit - result of comparison
);

always @ (posedge CLK)
  if (ALU_OUT == EXPECTED)
    RESULT = 1'b1;
  else
    begin
      RESULT = 1'b0;
      //display describes simulation mismatch and specifies the simulation time step when mismatch occurred
      //Sdisplay("At time %t, EXP = %b, ACT = %b, RESULT = %b", $time, EXPECTED, ALU_OUT, RESULT);
    end
end

endmodule

```

This is mem.v.

```

`timescale 1ns / 1ps
`include "MY_HEADER.txt"

module MEM(ADDR, DATA_FRAME, CLK, EN);
  //inputs
  input CLK, EN;
  input [ADDR-1:0] ADDR;

  //Output
  output reg [WIDTH-1:0] DATA_FRAME;

  always @ (posedge CLK)
    if (EN)
      case (ADDR)
        3'b000: DATA_FRAME = 17'b0010_0100_0_0000_0010;
        3'b001: DATA_FRAME = 17'b0010_0100_1_0000_0011;
        3'b010: DATA_FRAME = 17'b0010_0100_0_0001_0110;
        3'b011: DATA_FRAME = 17'b0010_0100_1_0010_1110;
        3'b100: DATA_FRAME = 17'b0011_0101_0_0111_1100;
        3'b101: DATA_FRAME = 17'b0010_0101_0_0101_0111;
        3'b110: DATA_FRAME = 17'b0000_0000_0_0000_0000;
        3'b111: DATA_FRAME = 17'b0000_0000_0_0000_0000;
        default: DATA_FRAME = 17'bx;
      endcase
end

endmodule

```

This is MY_HEADER.txt.

```

`define WIDTH 17
`define ADDR 3

```

IV. DISCUSSION & CONCLUSION

The purpose of this lab was to bring together all of the modules from the previous labs together and create a simple calculator. This calculator is pre-programmed with the arithmetic and logical operations with an expected output which the user give. The actual results are compared and if the calculator worked properly, the output is a high 1. Students now know how to design, build, test, and synthesis a circuit by using verilog HDL language.

Personally, I was happy to have worked on this final project with my partner, Tim Price. Together, we were able to quickly bring all of the modules together, hook them up, simulate, and synthesis the project to the Spartan 3E board. We had some stumbling blocks along the way, but nothing too sever. The one module which was giving us most hassle was the `CNTRL_FSM` module. There were all sorts of strange things it was doing, and we had to modify it a bit from our original one that we did in the previous lab. One in particular that I can remember was the `RST` pin being set to a high asserted reset. When we changed it to be a low asserted, most everything started to work properly.

There were some questions posed in the lab handout that I would like to address here in the conclusion:

- Using the Map Report, answer the following about your design:
 - Number of registers?
 - * 20
 - Number of 4-input LUTs?
 - * 40
 - Number of I/O blocks?
 - * 3
 - Number of global clocks?
 - * 1

Other conclusions that I can make is that the overall experience writing in verilog was much nicer and actually a lot of fun, which is something I didn't get with Circuit Maker and Cadence OrCAD. This was just a simple calculator and it demonstrated quite a bit of verilog capability. There's still a lot to learn about verilog and it will be exciting to continue learning it to build custom circuits into FPGAs.